

# Lecture 14

# Small-Signal Equivalent Circuit for FETs

Output signal from an amplifier using FET can be effectively modulated by small changes of input signal current. In this way it is possible to make small changes from the Q point.

Symbols:

The total quantities:  $i_D(t)$ ,  $v_{GS}(t)$

The dc point values:  $I_{DQ}$ ,  $V_{GSQ}$

The signal  $i_d(t)$ ,  $v_{gs}(t)$

$$v_{GS}(t) = V_{GSQ} + v_{gs}(t)$$

$$i_D(t) = I_{DQ} + i_d(t)$$

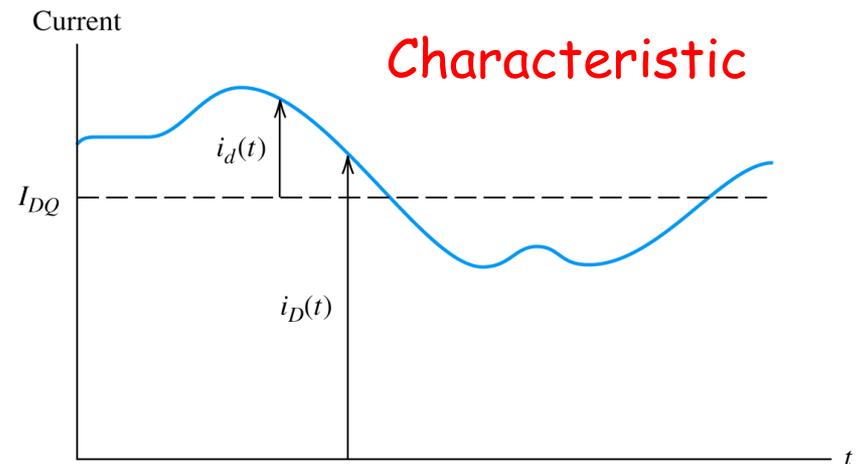


Figure 12.18 Illustration of the terms in Equation 12.15.

# Small-Signal Equivalent Circuit - Transconductance

Schematic

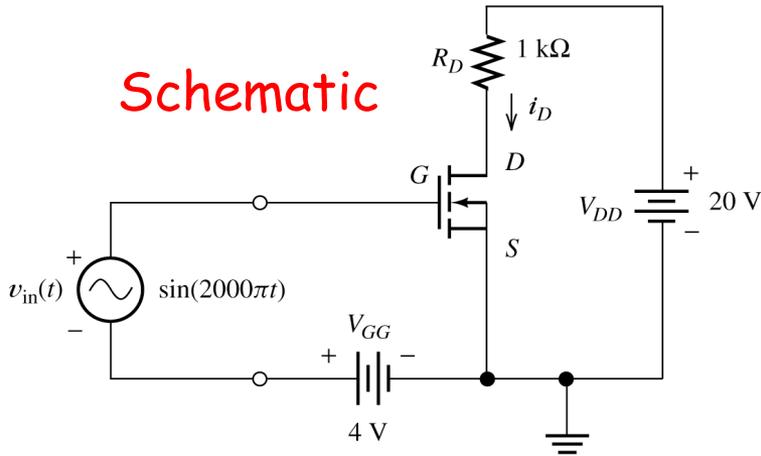


Figure 12.10 Simple NMOS amplifier circuit.

Analysis... (a little bit of math)

$$i_D = K(v_{GS} - V_{t0})^2$$

$$I_{DQ} + i_d(t) = K[V_{GSQ} + v_{gs}(t) - V_{t0}]^2$$

$$I_{DQ} + i_d(t) = K(V_{GSQ} - V_{t0})^2 + 2K(V_{GSQ} - V_{t0})v_{gs}(t) + Kv_{gs}^2(t)$$

We know that

$$I_{DQ} = K(V_{GSQ} - V_{t0})^2 *$$

Also we assume that

$$|v_{gs}(t)| \ll |(V_{GSQ} - V_{t0})|$$

# Small-Signal Equivalent Circuit - Transconductance

Schematic

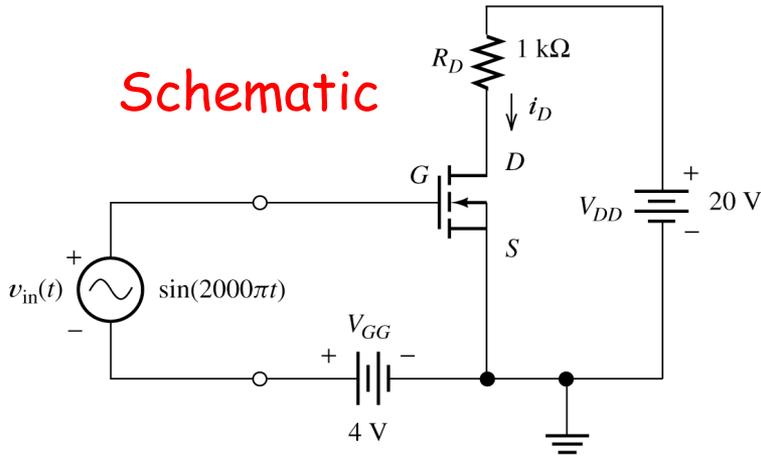


Figure 12.10 Simple NMOS amplifier circuit.

~~$$I_{DQ} + i_d(t) = K(V_{GSQ} - V_{t0})^2 + 2K(V_{GSQ} - V_{t0})v_{gs}(t) + Kv_{gs}^2(t)$$~~


We know that

$$I_{DQ} = K(V_{GSQ} - V_{t0})^2 *$$

Also we assume that

$$|v_{gs}(t)| \ll |(V_{GSQ} - V_{t0})|$$

Drain current generated  
by signal

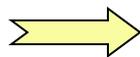

$$i_d(t) = 2K(V_{GSQ} - V_{t0})v_{gs}(t)$$

# Small-Signal Equivalent Circuit - Transconductance

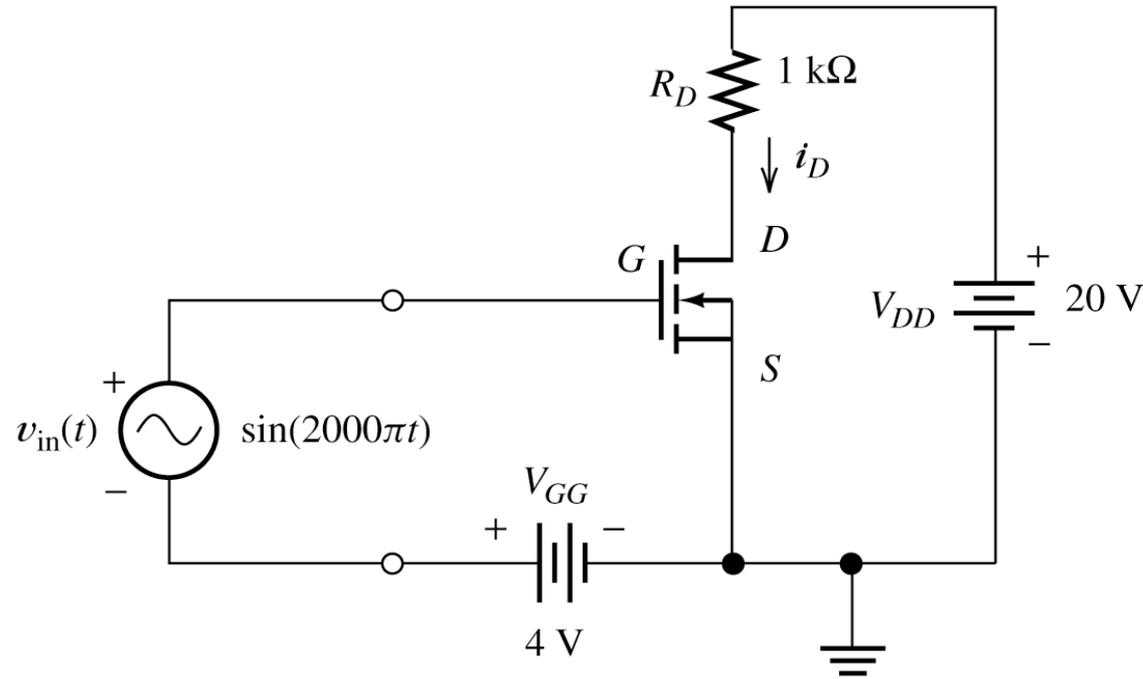


Figure 12.10 Simple NMOS amplifier circuit.

We define the transconductance as

$$g_m = \frac{i_d(t)}{v_{gs}(t)}$$

or

$$i_d(t) = g_m v_{gs}(t)$$

so

$$g_m = 2K(V_{GSQ} - V_{t0})$$

# Small-Signal Equivalent Circuit - Transconductance

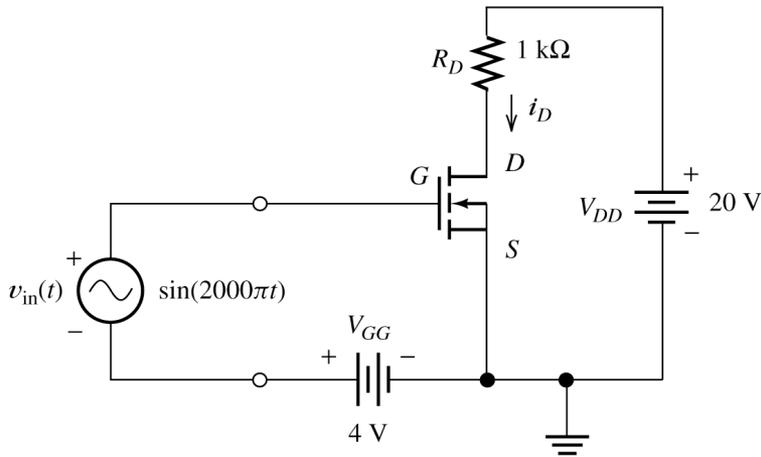


Figure 12.10 Simple NMOS amplifier circuit.

$$i_D = K(v_{GS} - V_{t0})^2$$

so

$$(v_{GS} - V_{t0}) = \sqrt{\frac{I_{DQ}}{K}}$$


Thus the  
transconductance

$$g_m = 2K(v_{GSQ} - V_{t0}) = 2\sqrt{KI_{DQ}}$$

# Small-Signal Equivalent Circuit - Transconductance
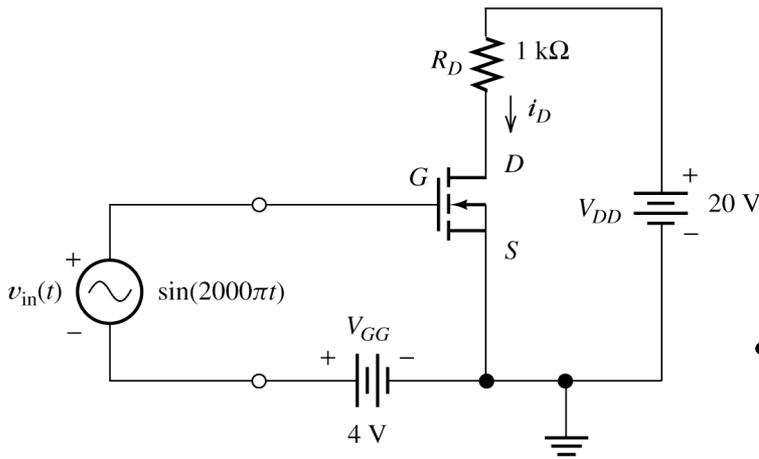
## Exercise

The transistor has  $KP=50\mu\text{A}/\text{V}^2$ ,  $V_{t0}=2\text{V}$ ,  $L=10\mu\text{m}$ , and  $W=400\mu\text{m}$




$$K = \left(\frac{W}{L}\right) \frac{KP}{2} = 1\text{mA}/\text{V}^2$$

$$g_m = 2K(V_{GSQ} - V_{t0}) = 2(4 - 2) = 4\text{mS}$$

Figure 12.10 Simple NMOS amplifier circuit.

# Small-Signal Equivalent Circuit

Also we assume that  $i_g(t) = 0$

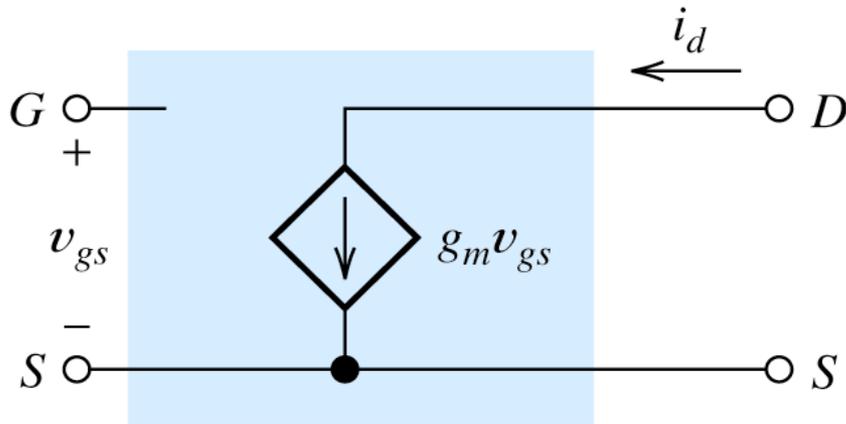

$$g_m = 2\sqrt{KI_{DQ}}$$

$$K = \left(\frac{W}{L}\right) \frac{KP}{2}$$

**Figure 12.19** Small-signal equivalent circuit for FETs.


Better performance is obtained with higher values of  $g_m$ . Please notice that  $g_m$  is proportional to the square root of the Q point drain current. Simply, we can increase  $g_m$  by choosing a higher value of  $I_{DQ}$ .

# More Complex Equivalent Circuits

For more accurate analyses of FET transistor we have to add more components to an equivalent circuit.

Small capacitance: for high response FET amplifiers

Drain resistor: account for the effect of  $v_{DS}$  on the drain current

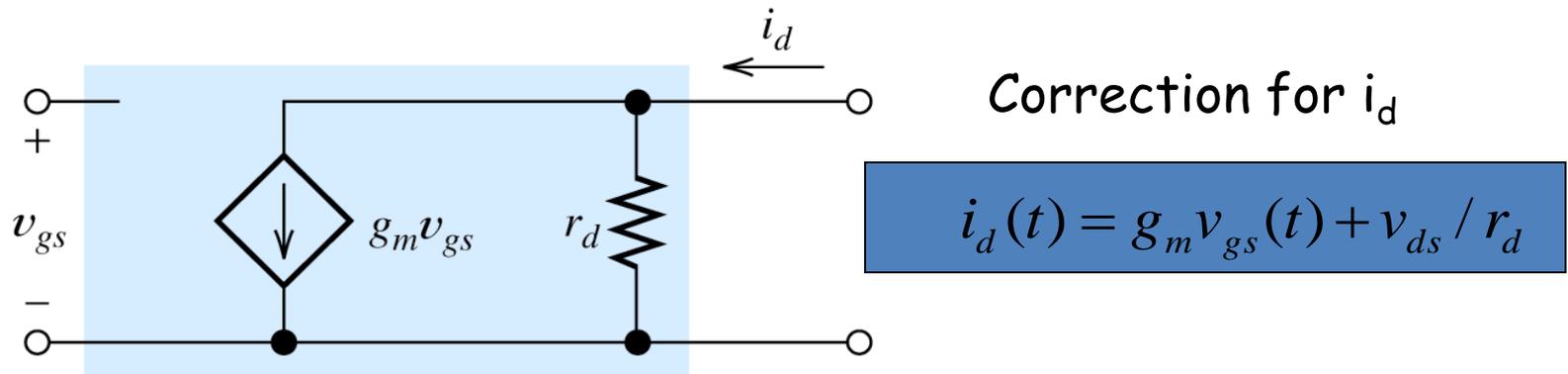

**Figure 12.20** FET small-signal equivalent circuit that accounts for the dependence of  $i_D$  on  $v_{DS}$ .

Please read section: Transconductance and ... pp.591  
Example 12.3