


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity dff is
    port(
        d : in STD_LOGIC;
        pr : in STD_LOGIC;
        cr : in STD_LOGIC;
        clk: in std_logic;
        q : out STD_LOGIC;
        qbar : out STD_LOGIC
    );
end dff;
architecture dff of dff is
begin
    process(clk,pr,cr)
    begin
        if (pr='0' and cr='1')then
            q <='1';

        elsif(pr='1'and cr='0')then
            q<='0';

        elsif(pr='1' and cr='1' and clk='0' and clk'event)then
            q<=d;
            qbar<= not d;
        end if;
    end process;

end dff;
```

Serial in serial out shift register

 

Data Flow style

```
Entity ssft_reg is
  Port ( din, clk, clr, pr: in bit;
         y: out bit );
End ssft_reg;
Architecture d_f of ssft_reg is
  Signal a: bit_vector (0 to 3);
  Begin
    a<= din & a(0) & a(1) & a(2)
    When clr='1' and pr= '1' and clk ='0' and clk'event
    Else
      "1111" when clr='1' and pr='0' else
      "0000" when clr='0' and pr='1' else
      Y<= a(3);
  End d_f;
```

Behavioral style

```
Entity ssft_reg is
Port ( din, clk, clr, pr: in bit; y: out bit );
End ssft_reg;
Architecture beh_f of ssft_reg is
Signal a(0), a(1), a(2) : bit;
Begin
  Process (clk, clr, pr)
    begin
      If (clr='1' and pr= '1' and clk ='0' and clk'event) then
        a(0) <= din;
        a(1)<= a(0);
        a((2)<= a(1);
        Y<= a(2);
      Elsif (clr='1' and pr='0' ) then
        a(0) <= '1';
        a(1)<= '1';
        a((2)<= '1';
        Y<= '1';
      Elsif (clr='0' and pr='1' ) then
        a(0) <= '0';
        a(1)<= '0';
        a((2)<= '0';
        Y<= '0';
      end if;  end process;
End beh f;
```

Structural style

```
Entity ssft_reg is
  Port (din, clk, clr, pr: in bit;
        y: out bit );
End ssft_reg;
Architecture str_f of ssft_reg is
  Component dff
    Port ( a, b, c, d: in bit; o1: out bit);
  End component;
  Signal a: bit_vector (0 to 2);
  Begin
    ff0: dff port map (din, clk, clr, pr, a(0));
    ff1: dff port map (a(0), clk, clr, a(1));
    ff2: dff port map (a(1), clk, clr, a(2));
    ff3: dff port map (a(2), clk, clr, y);
  End str_f;
```