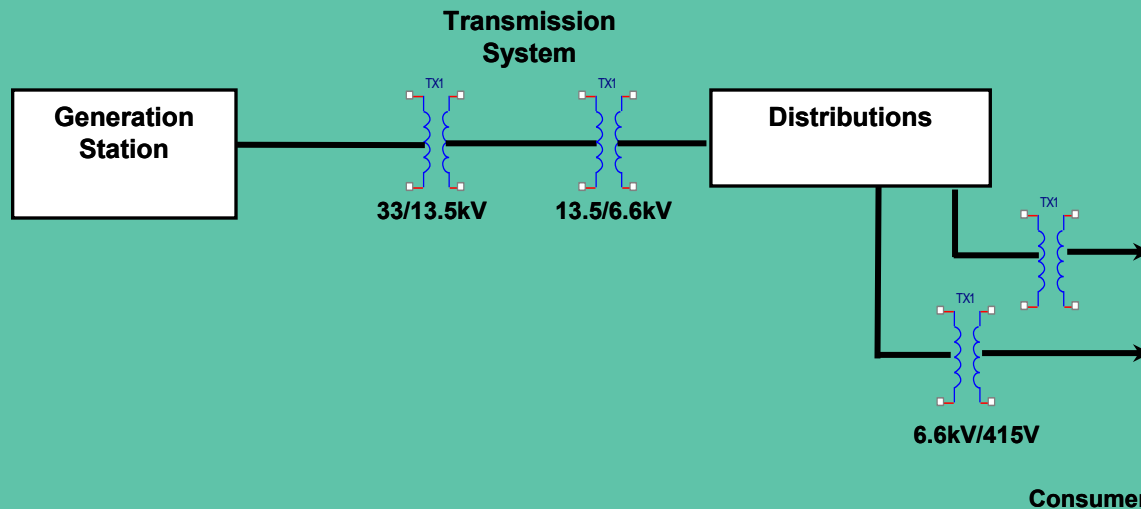



Introduction

- A transformer is a **static machines**.
- The word '**transformer**' comes form the word '**transform**'.
- Transformer is **not** an energy conversion device, but is a device that **changes** AC electrical power at one voltage level into AC electrical power at another voltage level through the action of magnetic field, without a change in frequency.
- It can be either to **step-up** or **step down**.



Ideal Transformer

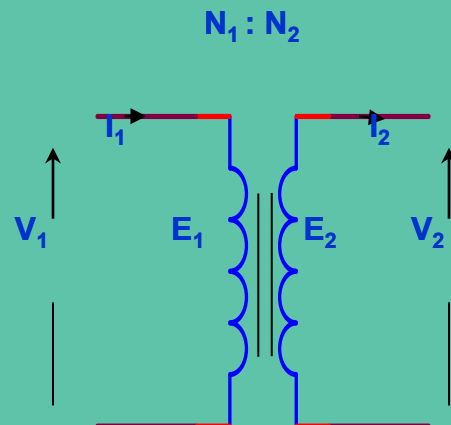- An ideal transformer is a transformer **which has no losses**, i.e. its winding has no ohmic resistance, no magnetic leakage, and therefore no $I^2 R$ and core losses.
- However, it is **impossible** to realize such a transformer in practice.
- Yet, the **approximate characteristic of ideal transformer will be used in characterizing the practical transformer.**



V_1 – Primary Voltage

V_2 – Secondary Voltage

E_1 – Primary induced Voltage

E_2 – secondary induced Voltage



$N_1:N_2$ – Transformer ratio

Transformer Construction

- Two types of iron-core construction:



- a) Core - type construction
- b) Shell - type construction

- Core - type construction

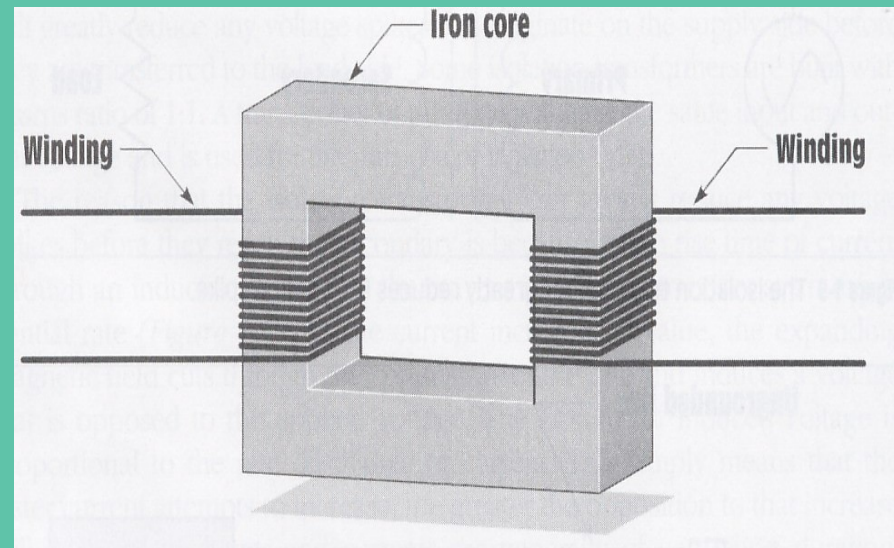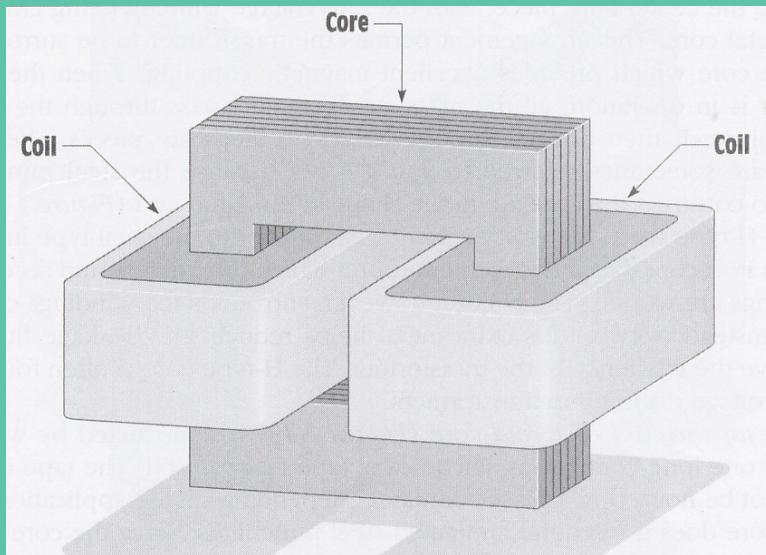

Transformer Construction

- Shell - type construction

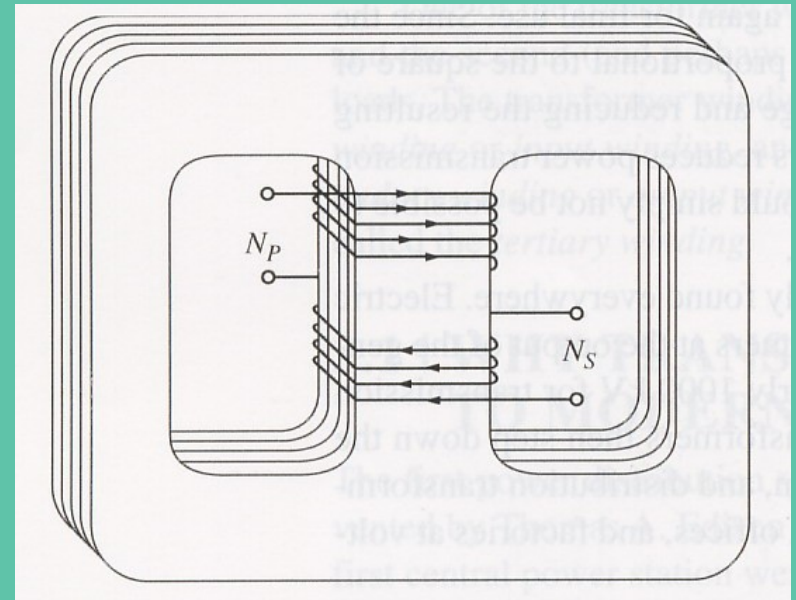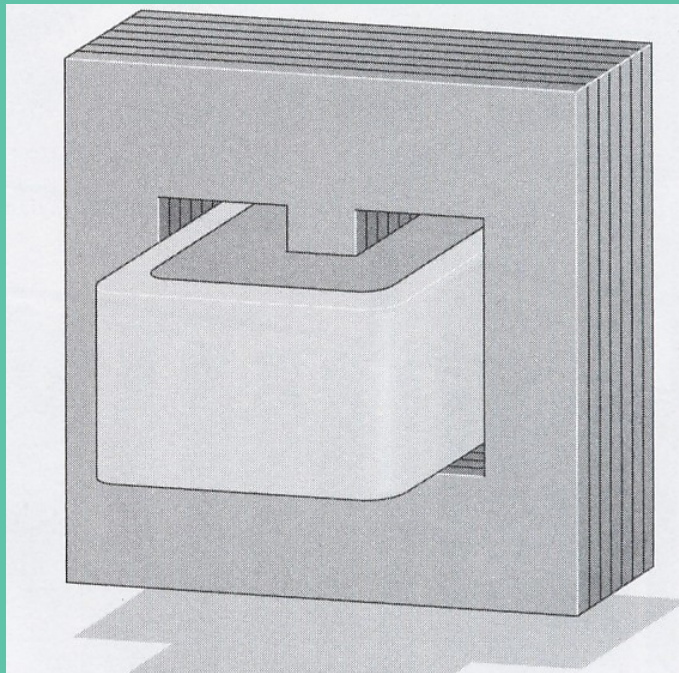

Transformer Equation

- Faraday's Law states that,
 - If the flux passes through a coil of wire, a voltage will be induced in the turns of wire. This voltage is directly proportional to the rate of change in the flux with respect of time.

$$V_{ind} = Emf_{ind} = - \frac{d\Phi(t)}{dt}$$

Lenz's Law

If we have N turns of wire,

$$V_{ind} = Emf_{ind} = -N \frac{d\Phi(t)}{dt}$$

Transformer Equation

■ For an ac sources,

■ Let $V(t) = V_m \sin \omega t$

$$i(t) = i_m \sin \omega t$$

Since the flux is a sinusoidal function;

Then:

Therefore: $\Phi(t) = \Phi_m \sin \omega t$

$$\begin{aligned} V_{ind} = Emf_{ind} &= -N \frac{d\Phi_m \sin \omega t}{dt} \\ &= -N\omega\Phi_m \cos \omega t \end{aligned}$$

Thus:

$$V_{ind} = Emf_{ind(max)} = N\omega\Phi_m = 2\pi f N\Phi_m$$

$$Emf_{ind(rms)} = \frac{N\omega\Phi_m}{\sqrt{2}} = \frac{2\pi f N\Phi_m}{\sqrt{2}} = 4.44 f N\Phi_m$$

Transformer Equation

- For an ideal transformer

$$E_1 == 4.44 f N_1 \Phi_m$$

$$E_2 == 4.44 f N_2 \Phi_m \quad \dots\dots\dots (i)$$

- In the equilibrium condition, both the input power will be equaled to the output power, and this condition is said to ideal condition of a transformer.

$$\textit{Input power} = \textit{output power}$$

$$V_1 I_1 \cos \theta = V_2 I_2 \cos \theta$$

$$\therefore \frac{V_1}{V_2} = \frac{I_2}{I_1}$$

- From the ideal transformer circuit, note that,

$$E_1 = V_1 \textit{ and } E_2 = V_2$$

- Hence, substitute in (i)

Transformer Equation

$$\text{Therefore, } \frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = a$$

Where, 'a' is the **Voltage Transformation Ratio**; which will determine whether the transformer is going to be step-up or step-down

For $a > 1 \longrightarrow E_1 > E_2$

For $a < 1 \longrightarrow E_1 < E_2$

Transformer Rating

- Transformer rating is normally written in terms of Apparent Power.
- Apparent power is actually the product of its rated current and rated voltage.

$$VA = V_1 I_1 = V_2 I_2$$

- Where,
 - I_1 and I_2 = rated current on primary and secondary winding.
 - V_1 and V_2 = rated voltage on primary and secondary winding.
- Rated currents are actually the full load currents in transformer

Example

1. 1.5kVA single phase transformer has rated voltage of 144/240 V. Finds its full load current.

Solution

$$I_{1FL} = \frac{1500}{144} = \underline{\underline{10.45A}}$$

$$I_{2FL} = \frac{1500}{240} = \underline{\underline{6A}}$$

Example

2. A single phase transformer has 400 primary and 1000 secondary turns. The net cross-sectional area of the core is 60m^2 . If the primary winding is connected to a 50Hz supply at 520V, calculate:
- a) The induced voltage in the secondary winding
 - b) The peak value of flux density in the core

Solution

$$N_1=400 \quad V_1=520\text{V} \quad A=60\text{m}^2$$

$$N_2=1000 \quad V_2=?$$

Example 2 (Cont)

a) Know that,

$$\begin{aligned} a &= \frac{N_1}{N_2} = \frac{V_1}{V_2} \\ \frac{400}{1000} &= \frac{520}{V_2} \\ V_2 &= \underline{\underline{1300V}} \end{aligned}$$

b) Emf, $E = 4.44 fN\Phi_m$

$$= 4.44 fN[B_m \times A]$$

$$\text{known, } E_1 = 520V, E_2 = 1300V$$

$$E = 4.44 fN[B_m \times A]$$

$$520 = 4.44(50)(400)(B_m)(60)$$

$$B_m = \underline{\underline{0.976Wb / m^2}}$$

Example

3. A 25kVA transformer has 500 turns on the primary and 50 turns on the secondary winding. The primary is connected to 3000V, 50Hz supply. Find:
- a) Full load primary current
 - b) The induced voltage in the secondary winding
 - c) The maximum flux in the core

Solution

$$VA = 25kVA$$

$$N_1 = 500 \quad V_1 = 3000V$$

$$N_2 = 50 \quad V_2 = ?$$

Example 3 (Cont.)

a) Know that, $VA = V \times I$

$$I_{1FL} = \frac{VA}{V_1} = \frac{25 \times 10^3}{3000} = \underline{\underline{8.33A}}$$

b) Induced voltage,

$$a = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$I_2 = 500 \left(\frac{8.33}{50} \right) = 83.3A$$

$$E_2 = E_1 \frac{I_1}{I_2} = 3000 \left(\frac{8.33}{83.3} \right) = \underline{\underline{300V}}$$


c) Max flux

$$E = 4.44 fN\Phi$$

$$300 = 4.44(50)(50)\Phi$$

$$\Phi = \underline{\underline{27mWb}}$$

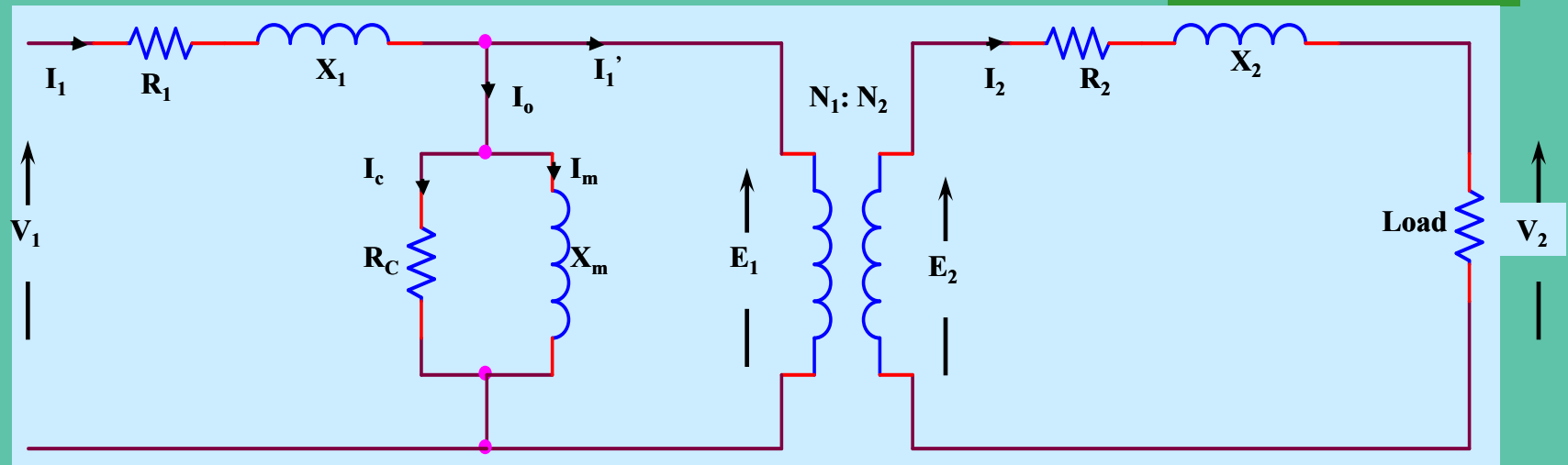Practical Transformer (Equivalent Circuit)



V_1 = primary supply voltage

V_2 = 2nd terminal (load) voltage

E_1 = primary winding voltage

E_2 = 2nd winding voltage

I_1 = primary supply current

I_2 = 2nd winding current

I_1' = primary winding current

I_0 = no load current

I_c = core current

I_m = magnetism current

R_1 = primary winding resistance

R_2 = 2nd winding resistance

X_1 = primary winding leakage reactance


X_2 = 2nd winding leakage reactance

R_c = core resistance

X_m = magnetism reactance

Single Phase Transformer (Referred to Primary)

■ Actual Method

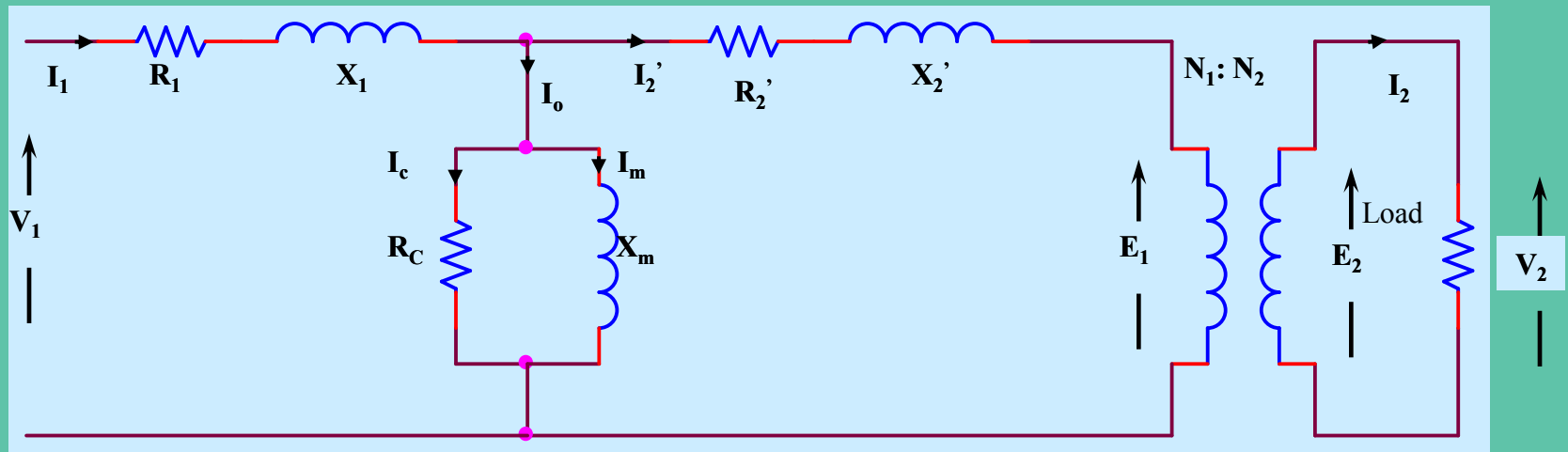

$$R_2' = \left(\frac{N_1}{N_2} \right)^2 R_2 \quad \text{OR} \quad R_2' = a^2 R_2$$


$$X_2' = \left(\frac{N_1}{N_2} \right)^2 X_2 \quad \text{OR} \quad X_2' = a^2 X_2$$

$$E_1 = V_2' = \left(\frac{N_1}{N_2} \right) V_2 \quad \text{OR} \quad V_2' = a V_2$$

$$I_2' = \frac{I_2}{a}$$

Single Phase Transformer (Referred to Primary)

■ Approximate Method

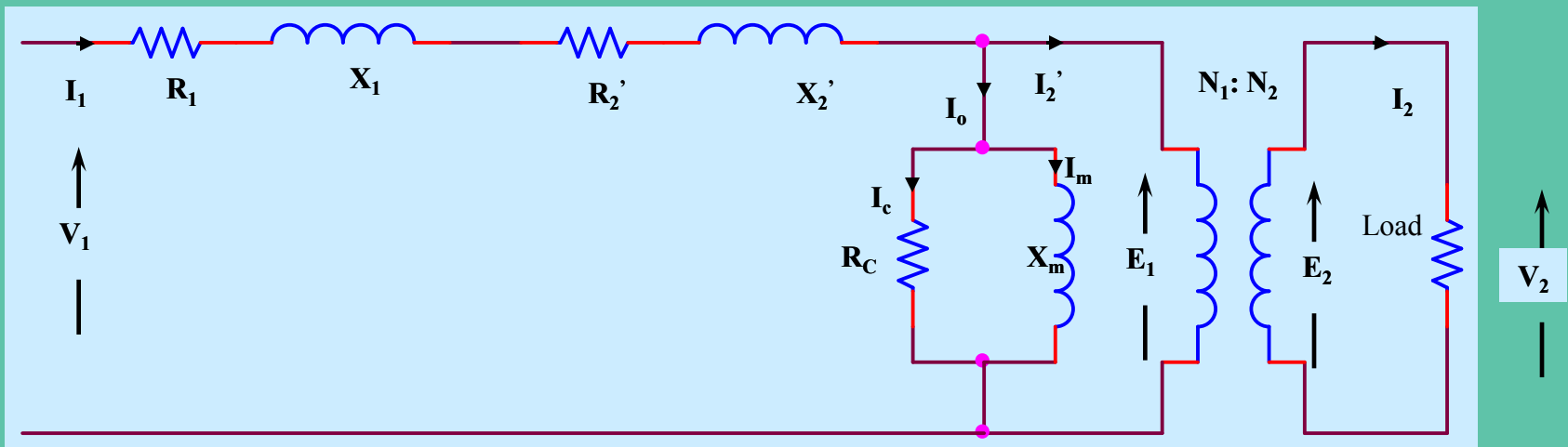

$$R_2' = \left(\frac{N_1}{N_2} \right)^2 R_2 \quad \text{OR} \quad R_2' = a^2 R_2$$


$$X_2' = \left(\frac{N_1}{N_2} \right)^2 X_2 \quad \text{OR} \quad X_2' = a^2 X_2$$

$$E_1 = V_2' = \left(\frac{N_1}{N_2} \right) V_2 \quad \text{OR} \quad V_2' = a V_2$$

$$I_2' = \frac{I_2}{a}$$

Single Phase Transformer (Referred to Primary)

■ Approximate Method

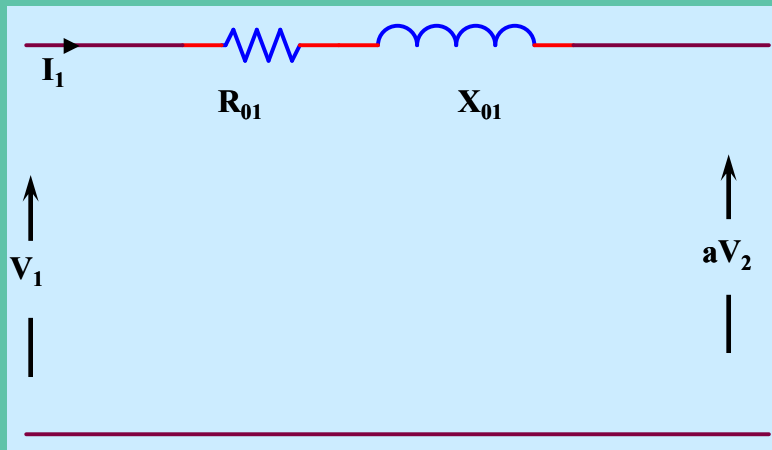

In some application, the excitation branch has a small current compared to load current, thus it may be neglected without causing serious error.

$$R_2' = \left(\frac{N_1}{N_2} \right)^2 R_2 \quad OR \quad R_2' = a^2 R_2$$


$$V_2' = \left(\frac{N_1}{N_2} \right) V_2 \quad OR \quad V_2' = a V_2$$

$$X_2' = \left(\frac{N_1}{N_2} \right)^2 X_2 \quad OR \quad X_2' = a^2 X_2$$

$$R_{01} = R_1 + R_2'$$
$$X_{01} = X_1 + X_2'$$

Single Phase Transformer (Referred to Secondary)

■ Actual Method

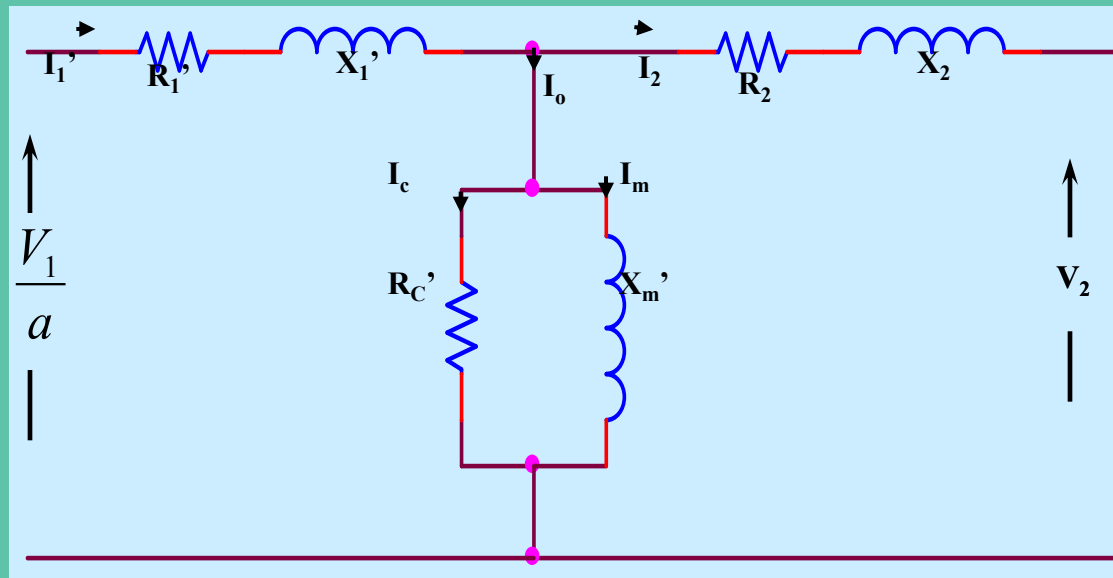


$$R_1' = \left(\frac{N_2}{N_1} \right)^2 R_1 \quad OR \quad R_1' = \frac{R_1}{a^2}$$

$$V_1' = \left(\frac{N_2}{N_1} \right) V_1 \quad OR \quad V_1' = \frac{V_1}{a}$$

$$X_1' = \left(\frac{N_2}{N_1} \right)^2 X_1 \quad OR \quad X_1' = \frac{X_1}{a^2}$$

Single Phase Transformer (Referred to Secondary)

■ Approximate Method

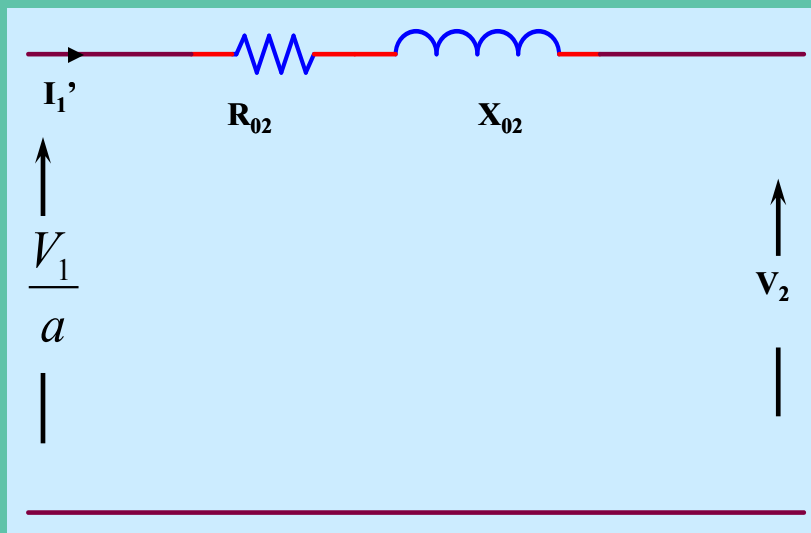

Neglect the excitation branch

$$R_{02} = R_1' + R_2$$

$$X_{02} = X_1' + X_2$$

$$V_1' = \left(\frac{N_2}{N_1} \right) V_1 \quad \text{OR} \quad V_1' = \frac{V_1}{a}$$

$$I_1' = a I_1$$

$$R_1' = \left(\frac{N_2}{N_1} \right)^2 R_1 \quad \text{OR} \quad R_1' = \frac{R_1}{a^2}$$

$$X_1' = \left(\frac{N_2}{N_1} \right)^2 X_1 \quad \text{OR} \quad X_1' = \frac{X_1}{a^2}$$

Example

4. For the parameters obtained from the test of 20kVA 2600/245 V single phase transformer, refer all the parameters to the high voltage side if all the parameters are obtained at lower voltage side.

$$R_c = 3.3\Omega, X_m = j1.5\Omega, R_2 = 7.5\Omega, X_2 = j12.4\Omega$$

Solution

Given

$$R_c = 3.3\Omega, X_m = j1.5\Omega,$$

$$R_2 = 7.5\Omega, X_2 = j12.4\Omega$$

Example 4 (Cont)

i) Refer to H.V side (primary)

$$a = \frac{E_1}{E_2} = \frac{V_1}{V_2} = \frac{2600}{245} = \underline{\underline{10.61}}$$

$$R_2' = (10.61)^2 (7.5) = \underline{\underline{844.65\Omega}},$$


$$X_2' = j(10.61)^2 (12.4) = \underline{\underline{1.396k\Omega}}$$

$$R_c' = (10.61)^2 (3.3) = \underline{\underline{371.6\Omega}},$$

$$X_m' = j(10.61)^2 (1.5) = \underline{\underline{j168.9 \Omega}}$$


Power Factor

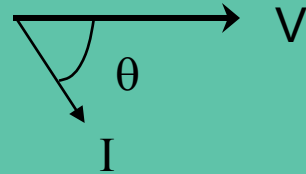- Power factor = angle between Current and voltage, $\cos \theta$



$\theta = -ve$

Lagging

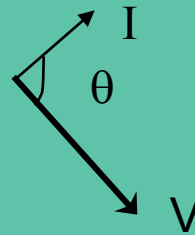

$\theta = +ve$

Leading



$\theta = 1$

unity

- Power factor always lagging for real transformer.

Example

5. A 10 kVA single phase transformer 2000/440V has primary resistance and reactance of 5.5Ω and 12Ω respectively, while the resistance and reactance of secondary winding is 0.2Ω and 0.45Ω respectively. Calculate:
- The parameter referred to high voltage side and draw the equivalent circuit
 - The approximate value of secondary voltage at full load of 0.8 lagging power factor, when primary supply is 2000V.

Example 5 (Cont)

Solution

$$R_1 = 5.5 \, \Omega, \quad X_1 = j12 \, \Omega$$

$$R_2 = 0.2 \, \Omega, \quad X_2 = j0.45 \, \Omega$$

i) Refer to H.V side (primary)

$$a = \frac{E_1}{E_2} = \frac{V_1}{V_2} = \frac{2000}{440} = \underline{\underline{4.55}}$$


$$R_2' = (4.55)^2 (0.2) = \underline{\underline{4.14 \, \Omega}},$$

$$X_2' = j(4.55)^2 0.45 = \underline{\underline{j9.32 \, \Omega}}$$

Therefore,

$$R_{01} = R_1 + R_2' = 5.5 + 4.13 = \underline{\underline{9.64 \, \Omega}}$$
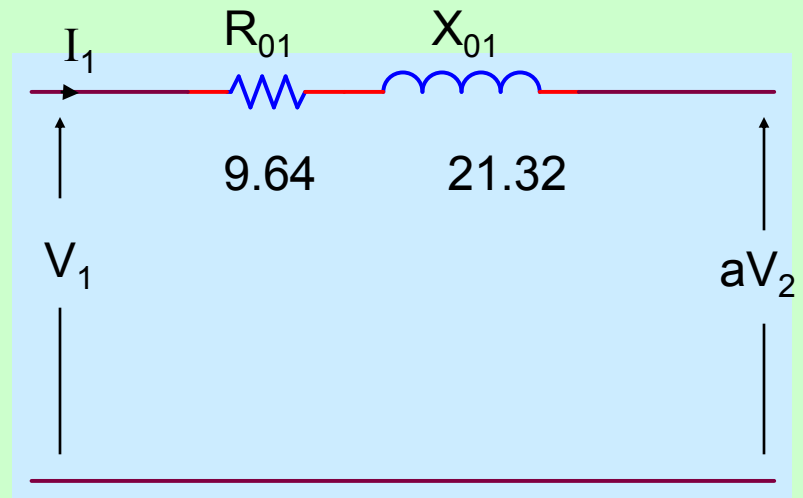
$$X_{01} = X_1 + X_2' = j12 + j9.32 = \underline{\underline{j21.32 \, \Omega}}$$



Example 5 (Cont.)

Solution

ii) Secondary voltage

$$\text{p.f} = 0.8$$

$$\cos \theta = 0.8$$

$$\theta = \underline{36.87^\circ}$$

$$\text{Full load,} \quad \longrightarrow \quad I_{FL_1} = \frac{10 \times 10^3 VA}{2000V} = \underline{5A}$$

From eqn. cct,

$$V_1 \angle 0^\circ = (R_{01} + jX_{01})(I_1 \angle -\theta^\circ) + aV_2$$

$$2000 \angle 0^\circ = (9.64 + j21.32)(5 \angle -36.87^\circ) + (4.55)V_2$$

$$V_2 = \underline{\underline{422.6 \angle 0.8^\circ}}$$

Transformer Losses

- Generally, there are two types of losses;
 - i. **Iron losses** :- occur in core parameters
 - ii. **Copper losses** :- occur in winding resistance

i. Iron Losses

$$P_{iron} = P_c = (I_c)^2 R_c = P_{open\ circuit}$$

ii. Copper Losses

$$P_{copper} = P_{cu} = (I_1)^2 R_1 + (I_2)^2 R_2 = P_{short\ circuit}$$

$$\text{or if referred, } P_{cu} = (I_1)^2 R_{01} = (I_2)^2 R_{02}$$

Transformer Efficiency

- To check the performance of the device, by comparing the output with respect to the input.
- The higher the efficiency, the better the system.

$$\begin{aligned}\text{Efficiency } \eta &= \frac{\text{Output Power}}{\text{Input Power}} \times 100\% \\ &= \frac{P_{out}}{P_{out} + P_{losses}} \times 100\% \\ &= \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + P_c + P_{cu}} \times 100\%\end{aligned}$$

Where $P_{cu} = P_{sc}$
 $P_c = P_{oc}$

$$\begin{aligned}\eta_{(fullload)} &= \frac{VA \cos \theta}{VA \cos \theta + P_c + P_{cu}} \times 100\% \\ \eta_{(load\ n)} &= \frac{nVA \cos \theta}{nVA \cos \theta + P_c + n^2 P_{cu}} \times 100\%\end{aligned}$$

Where, if $\frac{1}{2}$ load, hence $n = \frac{1}{2}$,
 $\frac{1}{4}$ load, $n = \frac{1}{4}$,
90% of full load, $n = 0.9$

Voltage Regulation

- The purpose of voltage regulation is basically to determine the percentage of voltage drop between no load and full load.
- Voltage Regulation can be determine based on 3 methods:
 - a) Basic Defination
 - b) Short – circuit Test
 - c) Equivalent Circuit

Voltage Regulation (Basic Definition)

- In this method, all parameter are being referred to primary or secondary side.
- Can be represented in either
 - Down – voltage Regulation

$$V.R = \frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\%$$

- Up – Voltage Regulation

$$V.R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

Voltage Regulation (Short – circuit Test)

- In this method, direct formula can be used.

$$V.R = \frac{V_{sc} \cos(\theta_{sc} \mp \theta_{p.f})}{V_1} \times 100\% \quad \longleftarrow \text{If referred to primary side}$$

$$V.R = \frac{V_{sc} \cos(\theta_{sc} \mp \theta_{p.f})}{V_2} \times 100\% \quad \longleftarrow \text{If referred to secondary side}$$

Note that:

‘–’ is for Lagging power factor

‘+’ is for Leading power factor

I_{sc} must equal to I_{FL}

Voltage Regulation (Equivalent Circuit)

- In this method, the parameters must be referred to primary or secondary

$$V.R = \frac{I_1 [R_{01} \cos \theta_{p.f} \pm X_{01} \sin \theta_{p.f}]}{V_1} \times 100\%$$

← If referred to primary side

$$V.R = \frac{I_2 [R_{02} \cos \theta_{p.f} \pm X_{02} \sin \theta_{p.f}]}{V_2} \times 100\%$$

← If referred to secondary side

Note that:

‘+’ is for Lagging power factor

‘−’ is for Leading power factor

j terms ~ 0

Example

6. In example 5, determine the Voltage regulation by using down – voltage regulation and equivalent circuit.

Solution

Down – voltage Regulation

Know that, $V_{2FL}=422.6V$

$$V_{2NL}=440V$$

Therefore,

$$\begin{aligned} V.R &= \frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\% \\ &= \frac{440 - 422.6}{440} \times 100\% \\ &= \underline{\underline{3.95\%}} \end{aligned}$$

Example 6 (Cont.)

Equivalent Circuit

$I_1=5\text{A}$ $R_{01}=9.64\Omega$ $X_{01}=21.32\Omega$ $V_1=2000\text{V}$, 0.8 lagging p.f

$$\begin{aligned} V.R &= \frac{I_1 [R_{01} \cos \theta_{p.f} \pm X_{01} \sin \theta_{p.f}]}{V_1} \times 100\% \\ &= \frac{5 [9.64(0.8) + 21.32(0.6)]}{2000} \times 100\% \\ &= \underline{\underline{5.12\%}} \end{aligned}$$

Example

7. A short circuit test was performed at the secondary side of 10kVA, 240/100V transformer. Determine the voltage regulation at 0.8 lagging power factor if

$$V_{sc} = 18V$$

$$I_{sc} = 100$$

$$P_{sc} = 240W$$

Solution

Check:

$$I_{FL_2} = \frac{VA}{V} = \frac{10000}{100} = 100A$$

$$I_{FL_2} = I_{sc},$$

Hence, we can use short-circuit method

$$V.R = \frac{V_{sc} \cos(\theta_{sc} \mp \theta_{p.f})}{V_2} \times 100\%$$

Example 7 (Cont.)

$$V.R = \frac{V_{sc} \cos(\theta_{sc} \mp \theta_{p.f})}{V_2} \times 100\%$$

Given $p.f = 0.8$

$$\text{Hence, } \theta_{p.f} = \cos^{-1} 0.8 = \underline{\underline{36.87^\circ}}$$

Know that,

$$P_{sc} = V_{sc} I_{sc} \cos \theta_{sc}$$

$$\begin{aligned} \theta_{sc} &= \cos^{-1} \left(\frac{P_{sc}}{V_{sc} I_{sc}} \right) \\ &= \cos^{-1} \left(\frac{240}{(18)(100)} \right) = \underline{\underline{82.34^\circ}} \end{aligned}$$

$$\begin{aligned} V.R &= \frac{18 \cos(82.34^\circ - 36.87^\circ)}{100} \times 100\% \\ &= \underline{\underline{12.62\%}} \end{aligned}$$

Example

8. The following data were obtained in test on 20kVA 2400/240V, 60Hz transformer.

$$V_{sc} = 72V$$

$$I_{sc} = 8.33A$$

$$P_{sc} = 268W$$

$$P_{oc} = 170W$$

The measuring instrument are connected in the primary side for short circuit test. Determine the voltage regulation for 0.8 lagging p.f. (use all 3 methods), full load efficiency and half load efficiency.

Example 8 (Cont.)

$$V.R = \frac{V_{sc} \cos(\theta_{sc} \mp \theta_{p.f})}{V_2} \times 100\%$$

Given $p.f = 0.8$

$$\text{Hence, } \theta_{p.f} = \cos^{-1} 0.8 = \underline{\underline{36.87^\circ}}$$

Know that,

$$P_{sc} = V_{sc} I_{sc} \cos \theta_{sc}$$

$$\begin{aligned} \theta_{sc} &= \cos^{-1} \left(\frac{P_{sc}}{V_{sc} I_{sc}} \right) \\ &= \cos^{-1} \left(\frac{268}{(72)(8.33)} \right) = \underline{\underline{63.4^\circ}} \end{aligned}$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{72}{8.33} = \underline{\underline{8.64\Omega}}$$

$\therefore Z_{sc} = 8.64 \angle 63.4^\circ = \underline{\underline{3.86 + j7.72}} = R_{01} + jX_{01}$ because connected to primary side.

Example 8 (Cont.)

1. Short Circuit method,
$$V.R = \frac{V_{sc} \cos(\theta_{sc} \mp \theta_{p.f})}{V_1} \times 100\%$$

$$V.R = \frac{72 \cos(63.4^\circ - 36.87^\circ)}{2400} \times 100\% = \underline{\underline{2.68\%}}$$

2. Equivalent circuit,
$$V.R = \frac{I_1 [R_{01} \cos \theta_{p.f} \pm X_{01} \sin \theta_{p.f}]}{V_1} \times 100\%$$

$$\frac{\frac{20000}{2400} [3.86(0.8) + 7.72(0.6)]}{2400} \times 100\% = \underline{\underline{2.68\%}}$$

Example 8 (Cont.)

3. Basic Defination,

$$V_1 = I_1 Z_{01} + aV_2$$

$$2400 \angle 0^\circ = \left(\frac{20000}{2400} \angle -36.87^\circ \right) (8.64 \angle 63.4^\circ) + \left(\frac{2400}{240} \right) V_2$$

$$V_2 = \underline{\underline{233.58 \angle 0.79^\circ \text{ V}}}$$

$$\begin{aligned} V.R &= \frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\% \\ &= \frac{240 - 233.58}{240} \times 100\% \\ &= \underline{\underline{2.68\%}} \end{aligned}$$

Example 8 (Cont.)

$$\eta_{(full\ load)} = \frac{(1)(20000)(0.8)}{(1)(20000)(0.8) + 170 + (1)^2(268)} \times 100\% = 97.34\%$$



$$\eta_{(half\ load)} = \frac{(0.5)(20000)(0.8)}{(0.5)(20000)(0.8) + 170 + (0.5)^2(268)} \times 100\% = 97.12\%$$

Measurement on Transformer

- There are two test conducted on transformer.
 - i. **Open Circuit Test**
 - ii. **Short Circuit test**
- The test is conducted to determine the parameter of the transformer.
- Open circuit test is conducted to determine magnetism parameter, R_c and X_m .
- Short circuit test is conducted to determine the copper parameter depending where the test is performed. If performed at primary, hence the parameters are R_{01} and X_{01} and vice-versa.

Open-Circuit Test

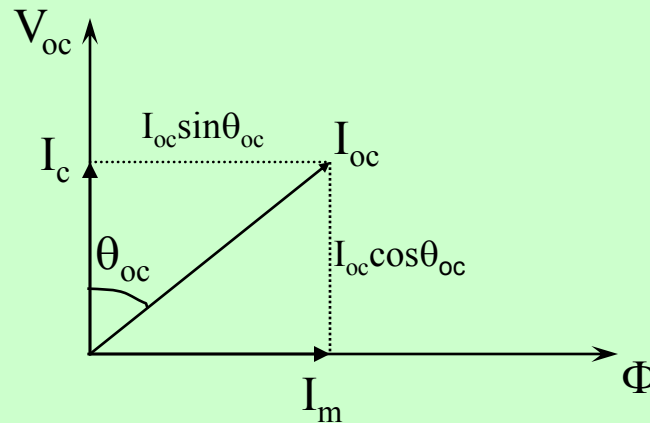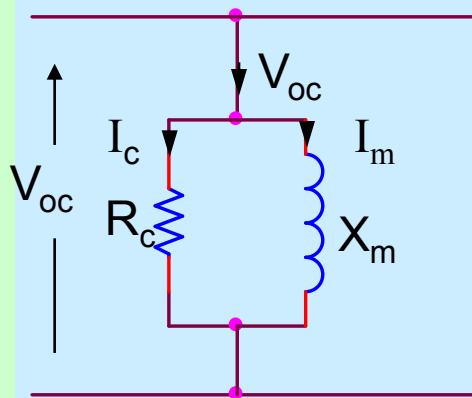- Measurement are at high voltage side
- From a given test parameters,



Note:

If the question asked parameters referred to Low voltage side, the parameters (R_c and X_m) obtained need to be referred to low voltage side

$$P_{oc} = V_{oc} I_{oc} \cos \theta_{oc}$$

$$\theta_{oc} = \cos^{-1} \left(\frac{P_{oc}}{V_{oc} I_{oc}} \right)$$

Hence,

$$I_c = I_{oc} \cos \theta_{oc}$$


$$I_m = I_{oc} \sin \theta_{oc}$$

Then, R_c and X_m ,

$$R_c = \frac{V_{oc}}{I_c}, \quad X_m = \frac{V_{oc}}{I_m}$$

Short-Circuit Test

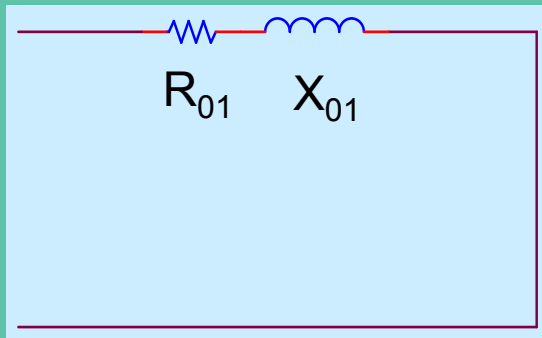- Measurement are at low voltage side
- If the given test parameters are taken on primary side, R_{01} and X_{01} will be obtained. Or else, vice-versa.



For a case referred to
Primary side

$$P_{sc} = V_{sc} I_{sc} \cos \theta_{sc}$$

$$\theta_{sc} = \cos^{-1} \left(\frac{P_{sc}}{V_{sc} I_{sc}} \right)$$

Hence,

$$Z_{01} = \frac{V_{sc}}{I_{sc}} \angle \theta_{sc}$$

$$Z_{01} = R_{01} + jX_{01}$$

Example

9. Given the test on 500kVA 2300/208V are as follows:

$$P_{oc} = 3800W$$

$$P_{sc} = 6200W$$

$$V_{oc} = 208V$$

$$V_{sc} = 95V$$

$$I_{oc} = 52.5A$$

$$I_{sc} = 217.4A$$

Determine the transformer parameters and draw equivalent circuit referred to high voltage side. Also calculate appropriate value of V_2 at full load, the full load efficiency, half load efficiency and voltage regulation, when power factor is 0.866 lagging.

[1392 Ω , 517.2 Ω , 0.13 Ω , 0.44 Ω , 202V, 97.74%, 97.59%, 3.04%]

Example 9 (Cont)


From Open Circuit Test,

$$P_{oc} = V_{oc} I_{oc} \cos \theta_{oc}$$

$$\theta_{oc} = \cos^{-1} \left(\frac{3800}{(52.5)(208)} \right) = \underline{\underline{69.6^\circ}}$$

$$\begin{aligned} I_c &= I_{oc} \cos \theta_{oc} \\ &= 52.5 \cos 69.6^\circ \\ &= \underline{\underline{18.26 A}} \end{aligned}$$
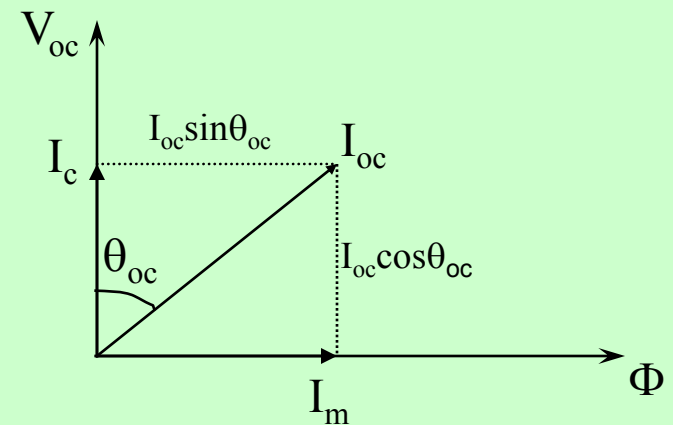
$$\begin{aligned} I_m &= I_{oc} \sin \theta_{oc} \\ &= 52.5 \sin 69.6^\circ \\ &= \underline{\underline{49.2 A}} \end{aligned}$$



Example 9 (Cont)

Since $V_{oc}=208V$

\therefore all reading are taken on the secondary side

$$R_c = \frac{V_{oc}}{I_c} = \frac{208}{18.26} = \underline{\underline{11.39\Omega}}$$

$$X_m = \frac{V_{oc}}{I_m} = \frac{208}{49.21} = \underline{\underline{4.23\Omega}}$$

Parameters referred to high voltage side,

$$R_c' = R_c \left(\frac{E_1}{E_2} \right)^2 = 11.39 \left(\frac{2300}{208} \right)^2 = \underline{\underline{1392\Omega}}$$

$$X_m' = X_m \left(\frac{E_1}{E_2} \right)^2 = 4.23 \left(\frac{2300}{208} \right)^2 = \underline{\underline{517.21\Omega}}$$

Example 9 (Cont)

From Short Circuit Test,

First, check the I_{sc}

$$I_{FL_1} = \frac{VA}{V_1} = \frac{500 \times 10^3}{2300} = \underline{\underline{217.4A}}$$

Since $I_{FL1} = I_{sc}$, \therefore all reading are actually taken on the primary side


$$P_{sc} = V_{sc} I_{sc} \cos \theta_{sc}$$

$$\theta_{sc} = \cos^{-1} \left(\frac{6200}{(95)(217.4)} \right) = \underline{\underline{72.53^\circ}}$$

$$\begin{aligned} Z_{01} &= \left(\frac{V_{sc}}{I_{sc}} \right) \angle \theta_{sc} \\ &= \left(\frac{95}{217.4} \right) \angle 72.53^\circ = 0.44 \angle 72.53^\circ \\ &= \underline{\underline{0.13 + j0.42\Omega}} \end{aligned}$$

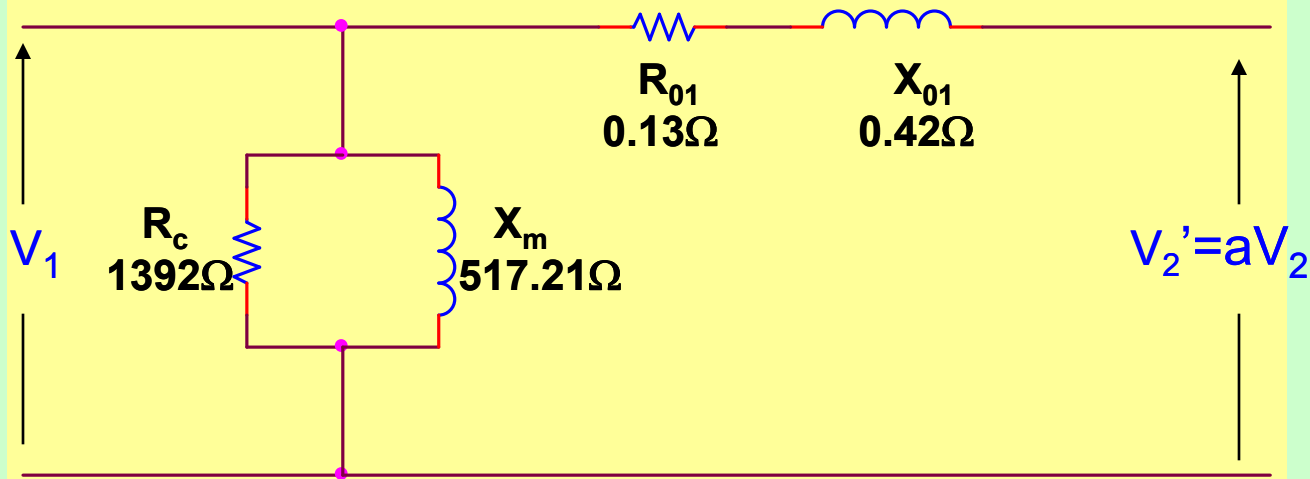Example 9 (Cont)

Equivalent circuit referred to high voltage side,



Example 9 (Cont)

Efficiency, η

$$\begin{aligned}\eta_{FL} &= \left[\frac{VA \cos \theta}{VA \cos \theta + P_{sc} + P_{oc}} \right] \times 100\% \\ &= \left[\frac{(500 \times 10^3)(0.866)}{(500 \times 10^3)(0.866) + 6200 + 3800} \right] \times 100\% \\ &= \underline{\underline{97.74\%}}\end{aligned}$$

$$\begin{aligned}\eta_{1/2L} &= \left[\frac{nVA \cos \theta}{nVA \cos \theta + n^2 P_{sc} + P_{oc}} \right] \times 100\% \\ &= \left[\frac{(0.5)(500 \times 10^3)(0.866)}{(0.5)(500 \times 10^3)(0.866) + (6200)(0.5)^2 + 3800} \right] \times 100\% \\ &= \underline{\underline{97.59\%}}\end{aligned}$$

Example 9 (Cont)

Voltage Regulation,

$$\begin{aligned} V.R &= \left[\frac{V_{sc} \cos[\theta_{sc} - \theta_{pf}]}{E_1} \right] \times 100\% \\ &= \left[\frac{(95) \cos[72.53 - 30]}{2300} \right] \times 100\% \\ &= \underline{\underline{3.04\%}} \end{aligned}$$